

CSED311 Lab2: RTL Design

Sangyoun Kwak
ksy109@postech.ac.kr


Contents

- Combinational logic
- Register-Transfer Level
- Finite State Machine
- Assignment
- Lab1 Demo

Combinational logic

- Represents Boolean function (time-independent)
- Output is a function of inputs only
- $\text{output} = f(\text{input})$

- Example: 4-to-1 mux

 

[3:0]in	sel	out
2'bxxx0	2'b00	0
2'bxxx1	2'b00	1
2'bxx0x	2'b01	0
2'bxx1x	2'b01	1
2'bx0xx	2'b10	0
2'bx1xx	2'b10	1
2'b0xxx	2'b11	0
2'b1xxx	2'b11	1

Combinational logic

- Implementation with Verilog (mux)


Using Assign	Using Always
<pre>module mux(in, sel, out); input [3:0] in; input [1:0] sel; output out; assign out = (sel == 2'b00) ? in[0] : (sel == 2'b01) ? in[1] : (sel == 2'b10) ? in[2] : in[3]; endmodule</pre>	<pre>module mux(in, sel, out); input [3:0] in; input [1:0] sel; output out; reg out; always @ (sel or in) begin if (sel == 2'b00) out <= in[0]; else if (sel == 2'b01) out <= in[1]; else if (sel == 2'b10) out <= in[2]; else out <= in[3]; end endmodule</pre>

Register-Transfer Level

- The design method to implement a **synchronous circuit** with a HDL (Hardware Description Language)
- Synchronous circuit consists of:
 - **Register**: a memory element synchronized by the clock signal
 - **Combinational logic**: logical function

RTL - Synchronous circuit example

- Toggler example

 

<Fig 1. "Register transfer level - example toggler" (Register-transfer level, Wikipedia, https://en.wikipedia.org/wiki/Register-transfer_level)>


```
module toggler(input clk, output out);  
    reg state;  
    wire comb;  
  
    assign comb = ~state;  
    assign out = state;  
  
    initial begin  
        state <= 0;  
    end  
  
    always @(posedge clk) begin  
        state <= comb;  
    end  
endmodule
```

Finite State Machine (FSM)

- Moore machine
- Mealy Machine


Finite State Machine (FSM)

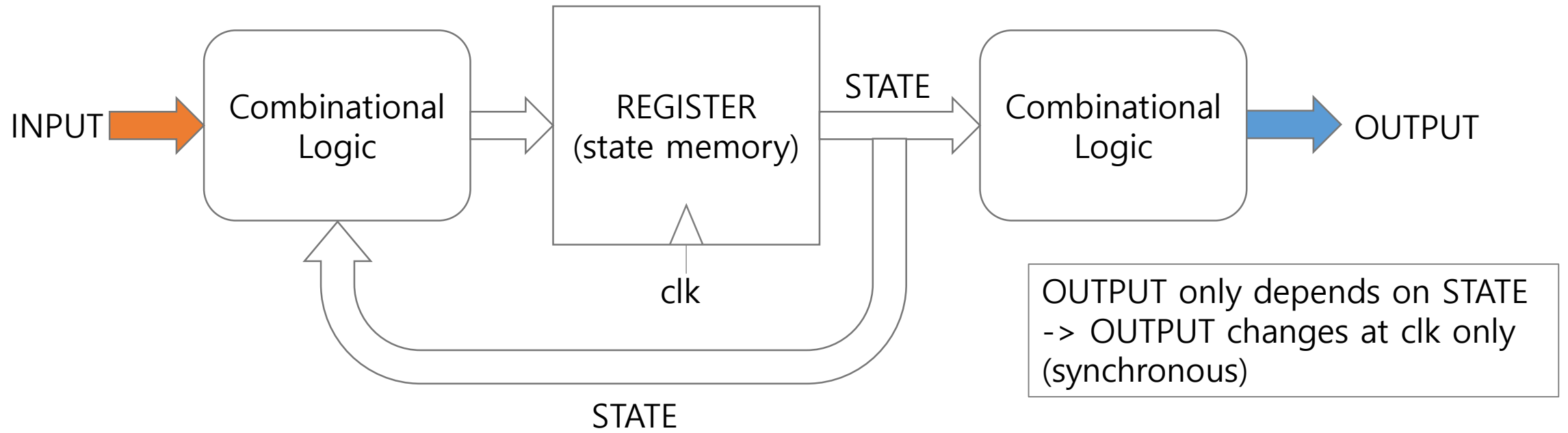- Moore Machine
 - Outputs only depend on the current state.




Finite State Machine (FSM)

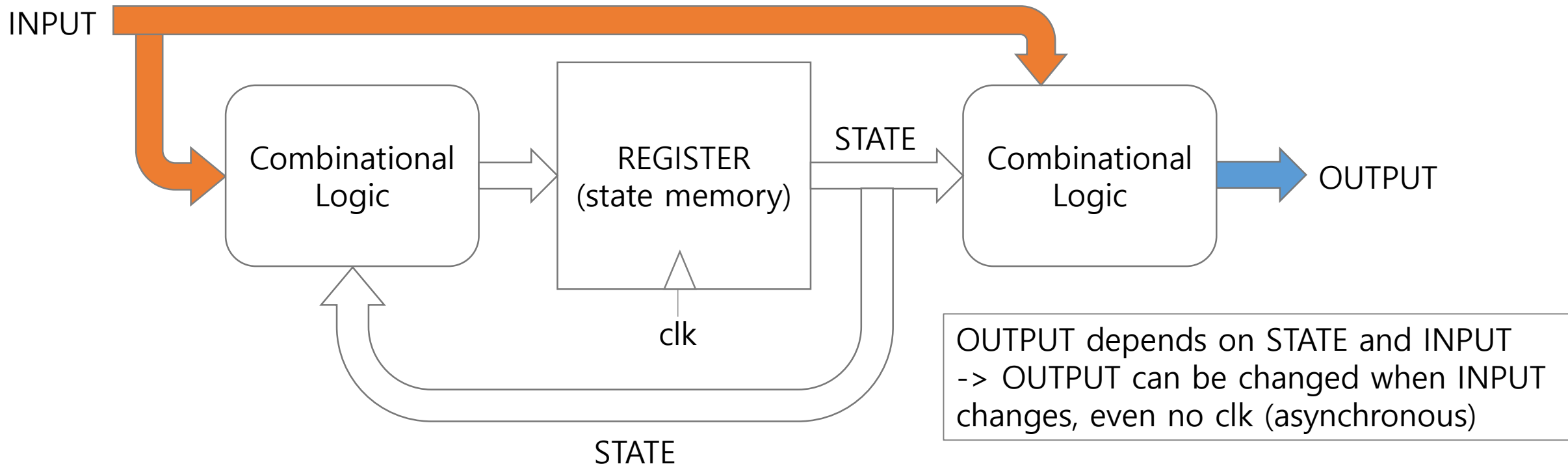- Mealy Machine
 - Outputs depend on the current state and the current inputs




Finite State Machine (FSM)

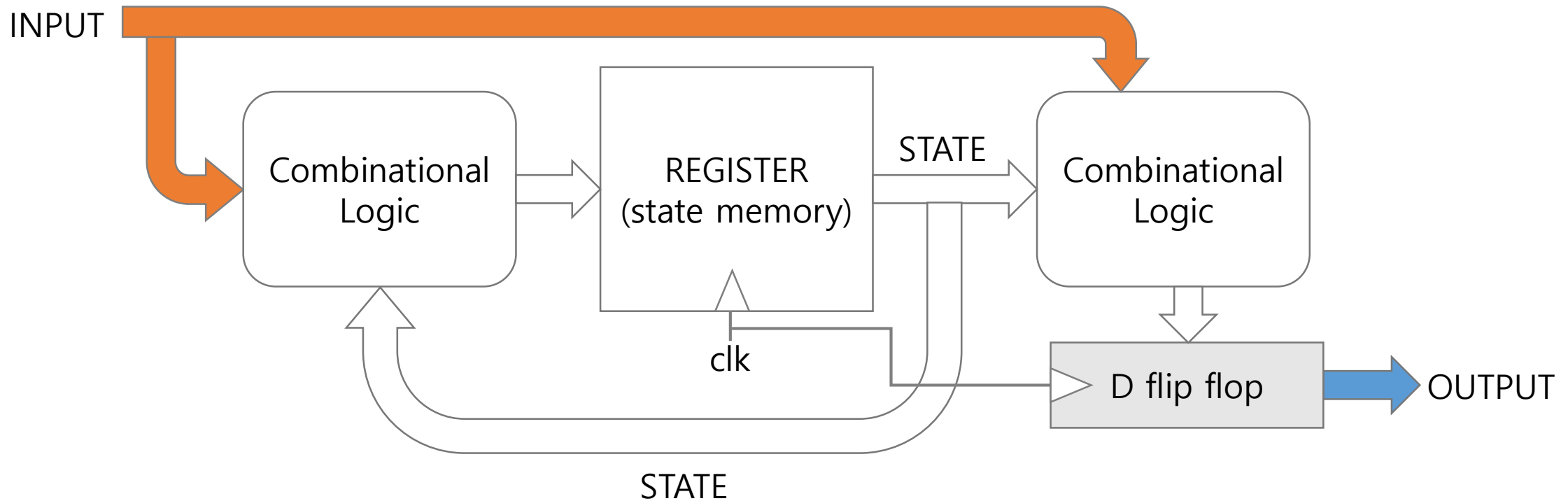- Mealy Machine
 - Mealy Machine can be made synchronous




FSM Code Structure

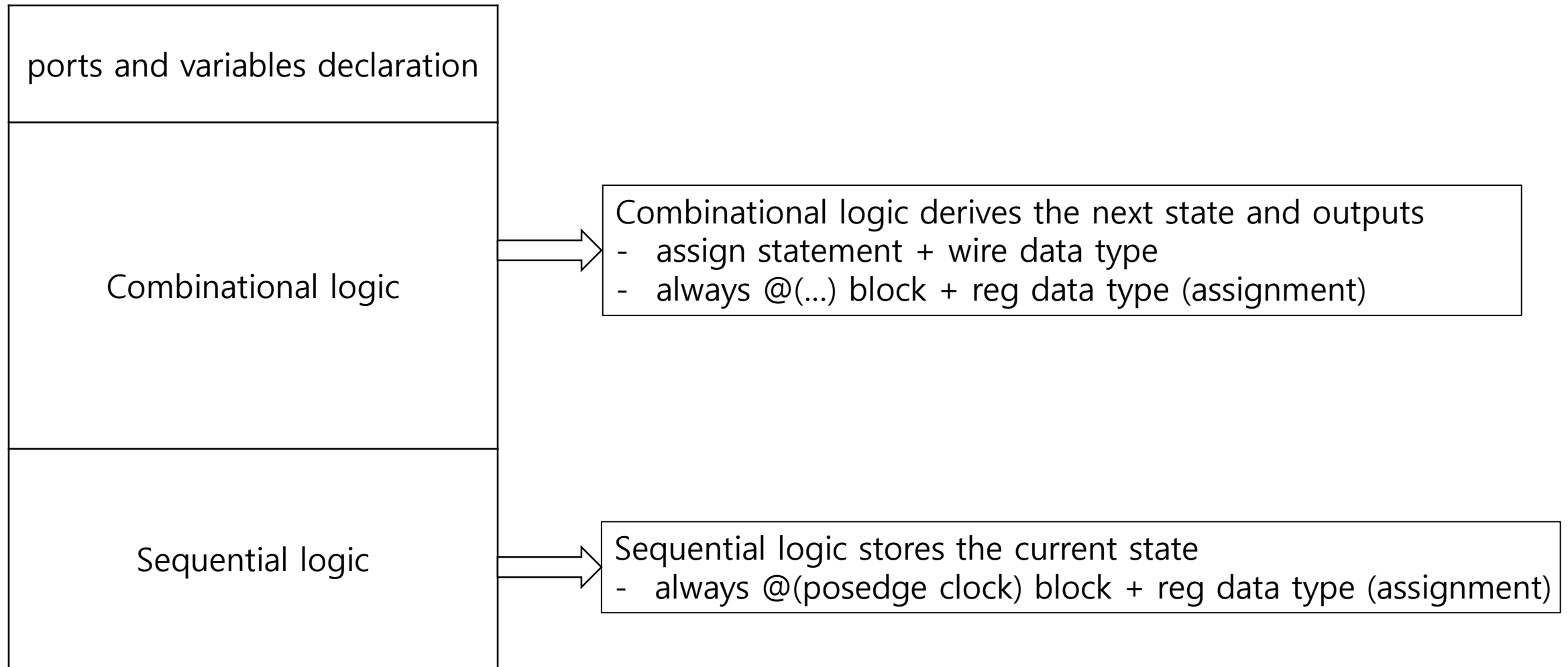

FSM Code Structure

❖ Example: Mealy Machine

 

Output: reg →

Example: Reduce 1's

Given a sequence of 0s and 1s, *change the first 1 of consecutive 1s into 0*

Examples:

0000**111**00 -> 0000**011**00

0**10101010** -> 0**00000000**

0**11001100** -> 0**01000100**

NS & Output
Calculation

CS
Calculation

z is output and z is in combinational logic part
-> asynchronous Mealy Machine

```
module mealy (Clock, w, Resetn, z);
  input Clock, w, Resetn ;
  output reg z ;
  reg CS, NS;
  parameter A = 1'b0, B = 1'b1;
  always @(w, CS)
    case (CS)
      A: if (w == 0)
          begin
            NS = A; z = 0;
          end
        else
          begin
            NS = B; z = 0;
          end
      B: if (w == 0)
          begin
            NS = A; z = 0;
          end
        else
          begin
            NS = B; z = 1;
          end
    endcase
  always @(posedge Clock, negedge Resetn)
    if (Resetn == 0)
      CS <= A;
    else
      CS <= NS;
endmodule
```

Combinational
(Blocking)

Sequential
(Non-Blocking)

Assignment

- Implement a simple vending machine RTL in Verilog
 - A simple Finite State Machine (FSM)
- Your vending machine should cover all use-cases (in the next slides)
- A testbench will be provided.

- Submit a report and code to LMS
 - Due date: 2019. 3. 12 6:30 pm
 - We will check the demo in the next lab session.

Assignment

- Vending machine interface

INPUT		
Signal	Description	Number of bit(s)
i_input_coin	Insert Coin	1 for each type of coins
i_select_item	Select Item	1 for each type of items
i_return_trigger	Return change	1
clk	clock	1
reset_n	reset	1

OUTPUT		
Signal	Description	Number of bit(s)
o_output_item	Indicate dispensed items	1 for each type of items
o_available_item	Indicate item availability	1 for each type of item
o_return_coin	Indicate type of coin (change)	1 for each type of coins

Assignment

- Vending machine use-case

Assumption: infinite item, change

Sequence

1. Insert money (available money unit: 100, 500, 1000 won)
2. Vending machine shows all available items where (item cost \leq current money && item count > 0)
- 3.a. Insert money within waiting time
 - 3.a.1. Go to 2
- 3.b. Select an item within waiting time
 - 3.b.a. Case1: the item is available
 - 3.b.a.1. The item is dispensed
 - 3.b.a.2. Go to 2
 - 3.b.b. Case 2: the item is unavailable
 - 3.b.b.1. Nothing happens. Waiting time is not reset.
- 3.c. No input within waiting time
 - 3.c.1 Return changes
- a*. Whenever press the return button
 - a*.1. Return changes
 - a*.2. Go to 1

Assignment

- Submission
 - Submit your assignment to LMS in a single zip file with filename:
 - Lab2_StudentID.zip
 - This zip file should contain:
 - Lab2_StudentID_Report.pdf
 - PDF file of your report
 - Lab2_StudentID_Code.zip
 - Zip file of your code (*.v)

Assignment tips

- If your modelsim is not displaying the output of \$display or \$monitor, then try using vending_machine_tb_f.v. (output will be written to output.txt)
- If your simulation keeps running, the testbench module is waiting for the output signals. (o_output_item or o_return_coin)
- If your vending machine code passes all tests, you will get the message "Passed = 10, Failed = 0".

Demo

You will be asked to

1. Show the TA that your implementation works
 - We will provide a testbench code for testing your implementation.
2. Answer some questions about your design and implementation
 - If you did your assignment well, you don't have to worry!

Reference

- "Register-transfer level", Wikipedia, last modified Jan 24, 2019, accessed Mar 03, 2019, https://en.wikipedia.org/wiki/Register-transfer_level